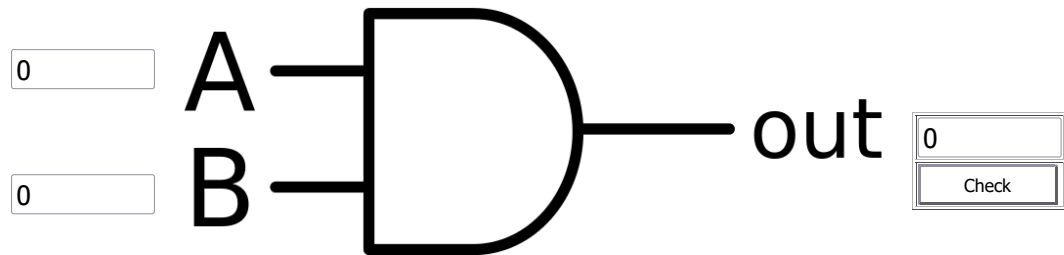


INSTRUCTIONS

Verification of truth table for AND gate



TRUTH TABLE

Serial No.	A	B	Output	Remarks
1	1	1	1	Correct
2	1	0	0	Correct
3	0	1	0	Correct
4	0	0	0	Correct