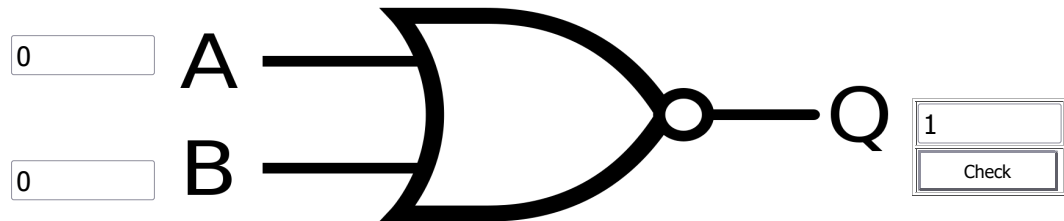


INSTRUCTIONS

Verification of truth table for NOR gate



TRUTH TABLE				Print
Serial No.	A	B	Output	Remarks
1	1	1	0	Correct
2	1	0	0	Correct
3	0	1	0	Correct
4	0	0	1	Correct

Reset