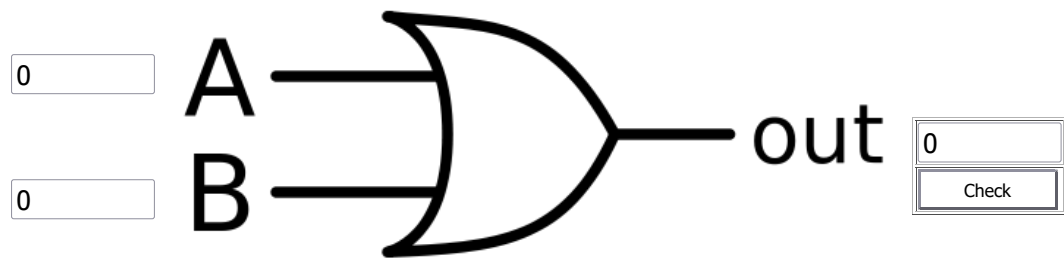


INSTRUCTIONS

Verification of truth table for OR gate



TRUTH TABLE

Serial No.	A	B	Output	Remarks
1	1	1	1	Correct
2	1	0	1	Correct
3	0	1	1	Correct
4	0	0	1	Incorrect
5	0	0	0	Correct