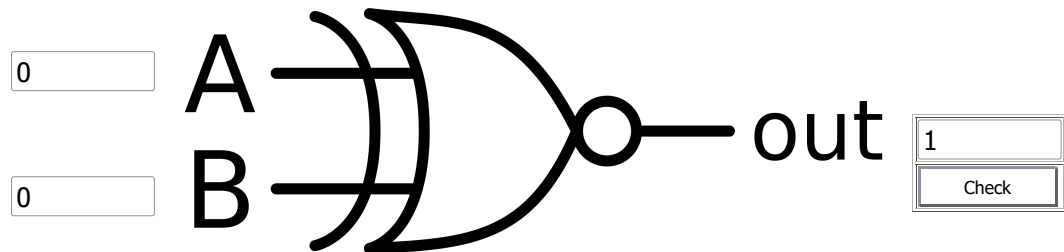


INSTRUCTIONS

Verification of truth table for XNOR gate



TRUTH TABLE

Print

Serial No.	A	B	Output	Remarks
1	1	1	1	Correct
2	1	0	1	Incorrect
3	1	0	0	Correct
4	0	1	0	Correct
5	0	0	1	Correct

Reset