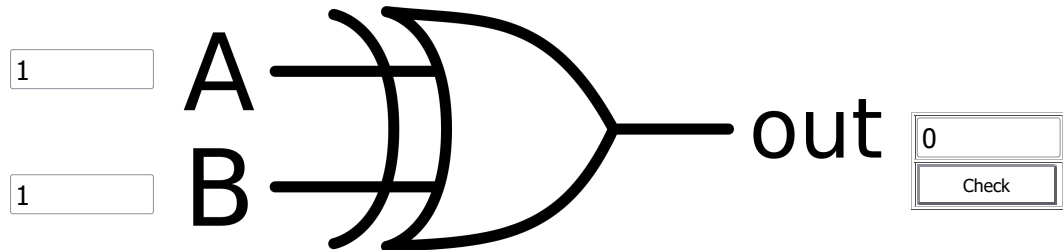


INSTRUCTIONS

Verification of truth table for XOR gate



TRUTH TABLE

Print

Serial No.	A	B	Output	Remarks
1	1	0	1	Correct
2	0	1	1	Correct
3	0	0	0	Correct
4	1	1	0	Correct

Reset